

High Voltage Linear Regulators and Constant Current Sources

Introduction


The LR8 and LR12 are high voltage 3-terminal adjustable linear regulators. Intended for operation directly off rectified AC mains, the LR8 operates at input voltages up to 450 volts, making it compatible with line voltages up to 230 VAC. The LR12, with its 100V maximum input, is ideal for 48V telecom applications. Their output voltage adjustability assures that they can be used in most any application.

Relevant specifications are shown in the table below.

LR8/LR12 Specifications

	LR8	LR12
Input Voltage Range	(V _{OUT} +12V) to 450V	(V _{OUT} +12V) to 100V
Output Voltage Range	1.2V to (V _{IN} - 12V)	1.2V to (V _{IN} - 12V)
Output Voltage Accuracy	±5%	±5%
Power Dissipation		
TO-92:	0.6W	0.6W
TO-243AA:	1.3W	—
SO-8:	—	1.8W
TO-252 (D-PAK):	2.0W	2.0W
Output Current	0.5 to 10mA	0.5 to 50mA
Load Regulation	3%	3%
Line Regulation	0.01%/V	0.01%/V
Supply Rejection	60dB typ @ 120Hz	60dB typ @ 120Hz
Minimum C _{OUT}	1µF	100nF

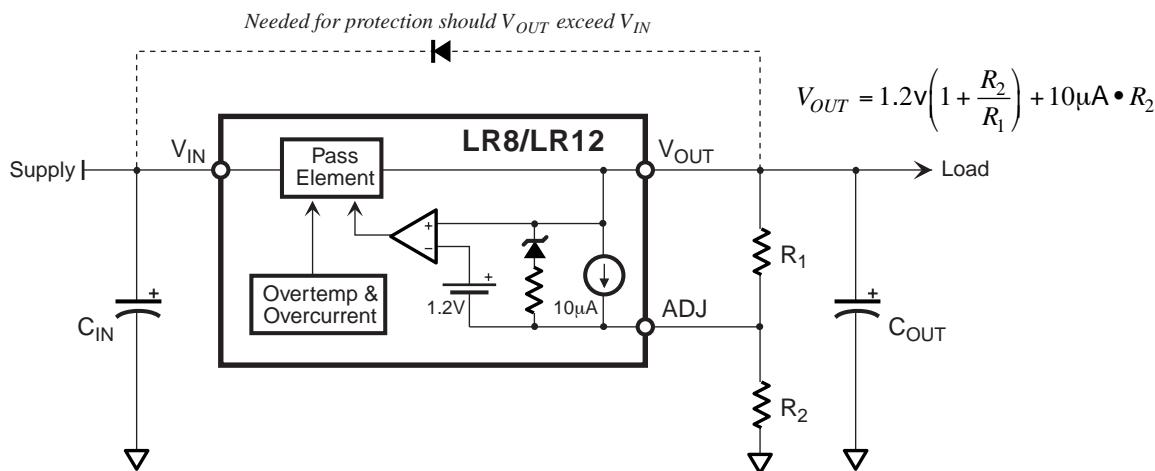LR8/LR12 Block Diagram and Typical Application



Operation

Except for their higher voltage rating, the LR8 and LR12 operate like any other 3-terminal adjustable linear regulator.

A simple resistive divider sets the output voltage while a capacitor at the output improves transient response and ensures regulator stability. When applicable, an input capacitor is required to provide energy storage for rectified AC.

Keeping in mind that the LR8/LR12 require at least a 12V difference between input and output for proper operation, the minimum value for C_{IN} is:


$$C_{IN} > I_{LOAD} \frac{t}{V_{IN(pk)} - V_{OUT} - 12V}$$

where I_{LOAD} = Load current
 t = Time between peaks of input waveform
 $V_{IN(pk)}$ = Peak input voltage
 V_{OUT} = Output voltage

Note that the LR8/LR12 require a minimum of 0.5mA load current for proper operation. The current through the resistive divider may be included as part of the minimum load.

Constant Current Operation

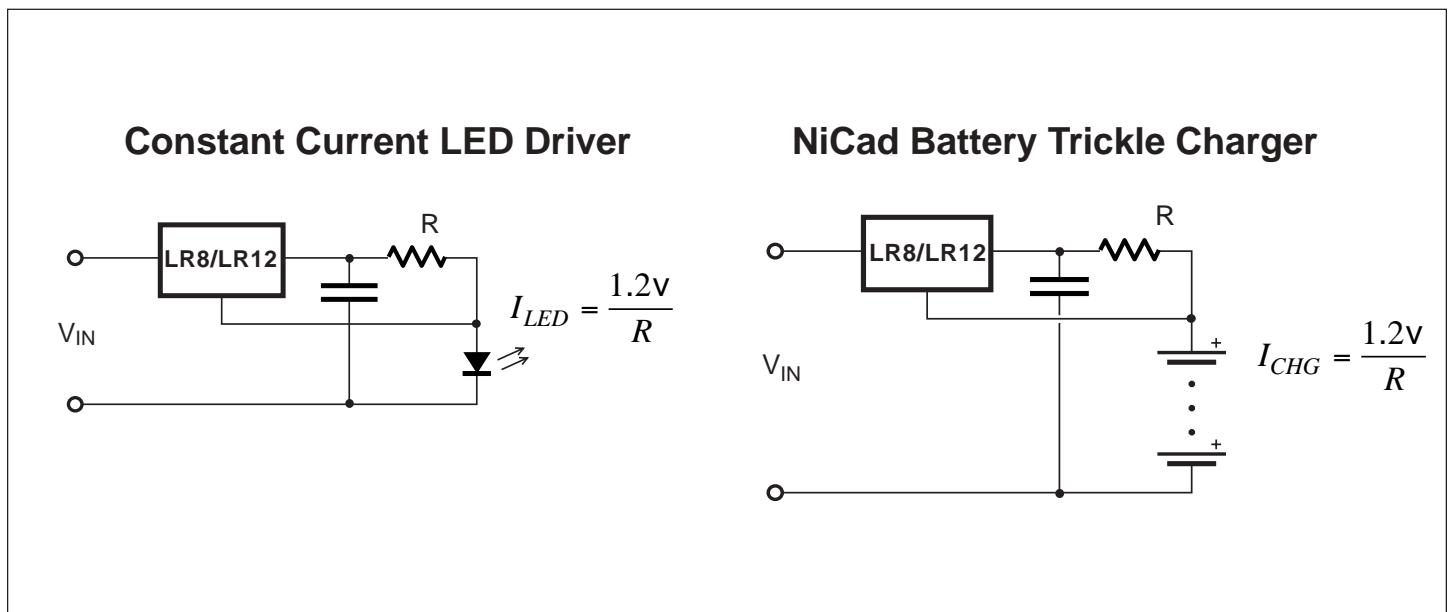The LR8/LR12 may be configured to provide a constant current output. The current is independent of both supply voltage and load impedance. Constant current operation finds application in driving LEDs and trickle-charging NiCad batteries, as shown below. The trickle charger is for applications that require battery backup (i.e. no cycling), such as emergency lights.




Start-up Circuit

The schematic below depicts a simplified off-line switching power supply using the LR8 for start-up. A similar circuit may be used for the LR12 for input voltages of less than 100V. When V_{BOOT} rises above the LR8's output voltage, the LR8 goes into standby mode, consuming very little current. All current is then supplied from the bootstrap circuit rather than from the high voltage source, increasing overall efficiency.

The output voltage of the LR8 should be set high enough above the minimum operating voltage of the PWM controller, yet low enough to ensure the bootstrap circuit takes over after start-up.




With 230VAC input, instantaneous power dissipation can reach 3.25W (325Vpk * 10mA). This level exceeds the LR8's rating, but exists for only as long as it takes for the supply to bootstrap. Thermal mass will prevent die temperature from rising quickly. If boot time is short, die temperatures will not reach the overtemperature protection trip point. It is advisable to mount the LR8 on 2 oz. copper with an area of at least 2.5 square centimeters.

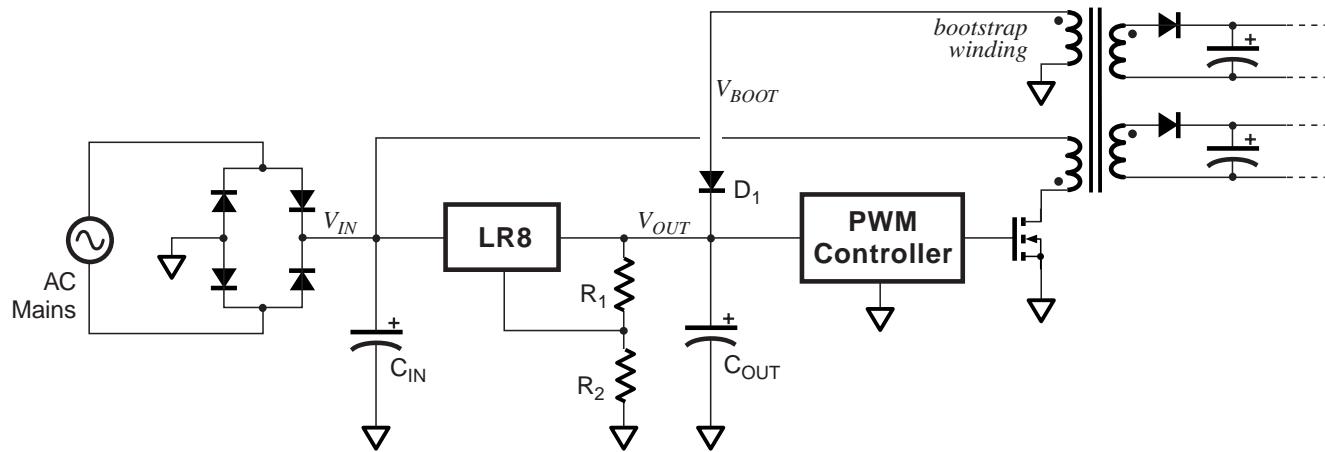Startup Current for Off-line Switching Power Supply



Comparison with Discrete Startup Implementations


The LR8 provides several advantages when compared with discretely implemented start-up circuits.

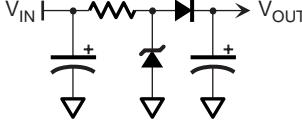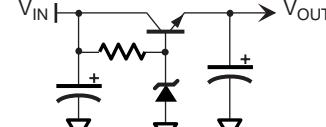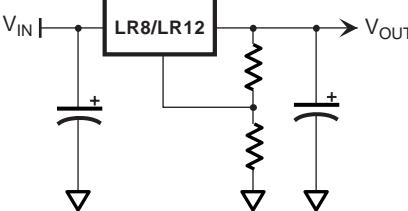Zener Implementation	Transistor Implementation	LR8/LR12 Implementation
		
Disadvantages		
<ul style="list-style-type: none"> <i>Inefficient</i> – Continues to draw current from high voltage source after supply has bootstrapped, resulting in inefficiencies <i>Poor dynamic range</i> – Bias must be set for minimum input voltage, resulting in high current drain at high input voltages Poor regulation No current limit No overtemperature protection In the Zener implementation, requires large power resistor and Zener 		Advantages <ul style="list-style-type: none"> LR8/LR12 goes into standby mode after supply has bootstrapped, drawing no current from high voltage input Good regulation Built-in current limiting Overtemperature protection

Exceeding LR8/LR12's Current Limit for Startup Applications

The LR8 has a built-in current limit of 10mA minimum, 50mA for the LR12. If the current drawn by the PWM controller exceeds this limit, the LR8/LR12 may still be used. To do this, the LR8/LR12's output capacitors supply a portion of the current until the power supply can bootstrap itself and the LR8/LR12 is no longer needed. The following figure graphically illustrates how this is accomplished.

Most PWM controllers have an undervoltage lockout (UVL) circuit or programmable start/stop voltages. When the voltage supplied to the PWM controller reaches the turn-on threshold, the controller begins operating and consuming current. If current exceeds the current limit for the LR8/LR12, the voltage at V_{OUT} begins to decay. With a large enough capacitor, the supply will bootstrap before voltage decays to the turn-off threshold.

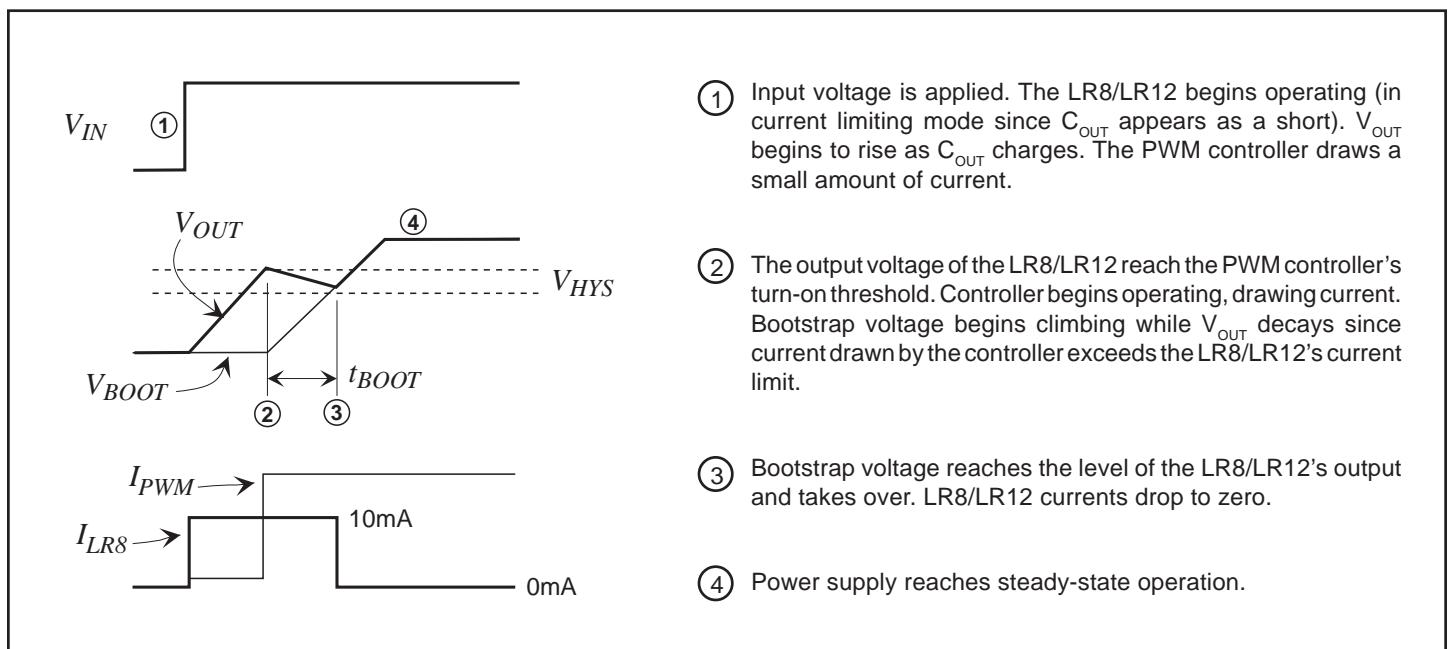

The minimum capacitance required for given boot-up time is given by the following equation:

$$C_{OUT} > t_{BOOT} \frac{I_{PWM} - I_{LIM}}{V_{HYS}}$$

where C_{OUT} = Capacitor at LR8/LR12 output
 t_{BOOT} = Time required for supply to bootstrap
 I_{PWM} = Current used by PWM controller
 I_{LIM} = LR8/LR12 current limit (LR8:10mA, LR12:50mA)
 V_{HYS} = PWM controller UVL hysteresis

Remember that this equation is valid only when PWM currents exceed the LR8/LR12's current limit.

Calculating Maximum Output Current

The LR8/12 have built-in current limiting, however, power dissipation may limit maximum continuous current to less than the built-in current limit. Power dissipation is given by:

$$P_{LR} = I_{OUT}(V_{IN} - V_{OUT})$$

This power dissipation will cause die temperature to rise above ambient (T_{amb}), the amount determined by the thermal resistance from junction to ambient (θ_{ja}). Since the LR8/12 have overtemperature protection that kicks-in as low as 125°C, junction temperature cannot exceed this amount.


$$\begin{aligned} T_j &= T_{amb} + \theta_{ja} P_{LR} \\ &= T_{amb} + \theta_{ja} \cdot I_{OUT}(V_{IN} - V_{OUT}) \end{aligned}$$

Rearranging the above equation yields a convenient equation that specifies maximum output current for given operating conditions. Remember that the output current cannot exceed built-in current limiting (10mA for LR8, 50mA for LR12).

$$I_{OUT(\max)} = \frac{T_{j(\max)} - T_{amb}}{\theta_{ja}(V_{IN} - V_{OUT})} \quad \text{where } T_{j(\max)} = 125^\circ\text{C}$$

If the maximum possible output current does not meet requirements, thermal resistance may be lowered by increasing the copper area used as a heat sink. In addition, a copper area on the other side of the PCB may be employed, connected by thermal vias.

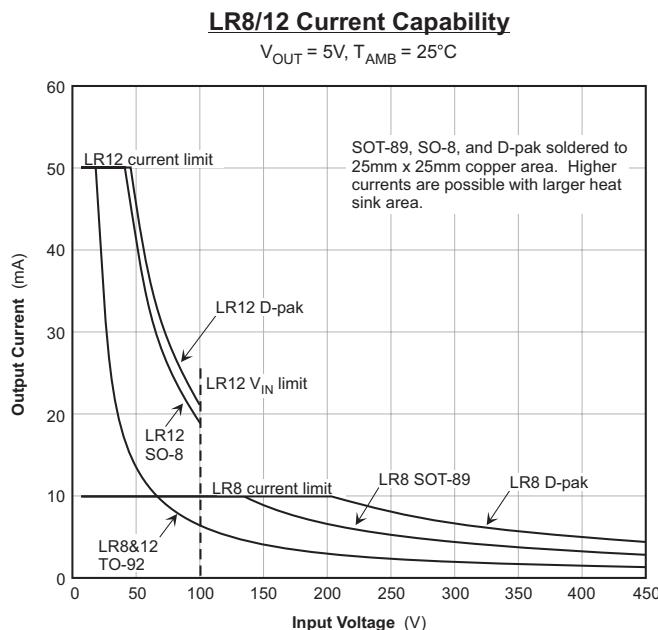As an example, the following graph shows the current capabilities of the LR8/12 at 25°C ambient with a 25mm x 25mm single-sided copper area heat sink for the surface mount devices.



Thermal Resistances

Pkg	θ_{jc}	θ_{ja}
TO-92	125°C/W	170°C/W
SOT-89	15°C/W	78°C/W*
SO-8	—	55°C/W*
D-Pak	6.25°C/W	50°C/W*

* When mounted to 25mm x 25mm copper area

06/16/03rev.3