

Current monitoring with the ZXCT1009 considering high voltage transients

Transients, also known as surges are changes in current or voltage which occur in short duration. These cause the power supply to operate outside what would be its normal operating condition boundaries.

Transients can be both internal and external and can not only damage components but also cause a complete system failure if the circuit doesn't have sufficient protection. Transients are such that they can cause progressive damage to components over a period of time. Internally generated transients can often be energy stored in inductive or capacitive elements which is released if operating conditions change. A transient is created every time an inductive element is switched within a circuit, for example a motor. Other transients can come from external sources such as lightning.


Typical internal transient sources include:

- Load dumps
- Inductive switching
- Ignition pulse

In circuits where a current needs to be measured accurately if transients are present, snubber circuits or expensive components can often be required, which increases component count.

The ZXCT1009 has the particular feature of being a three terminal device. A ground terminal is omitted from the ZXCT1009 which allows a voltage to be scaled to any reference potential. This is providing the reference is at least 2.5V below V_{in} and the device is within its normal operating range. This allows an additional resistor to be inserted between R_{out} and the ZXCT1009, when a current is required to be measured where voltage transients are present.

Figure 1 Current measurement into a solenoid

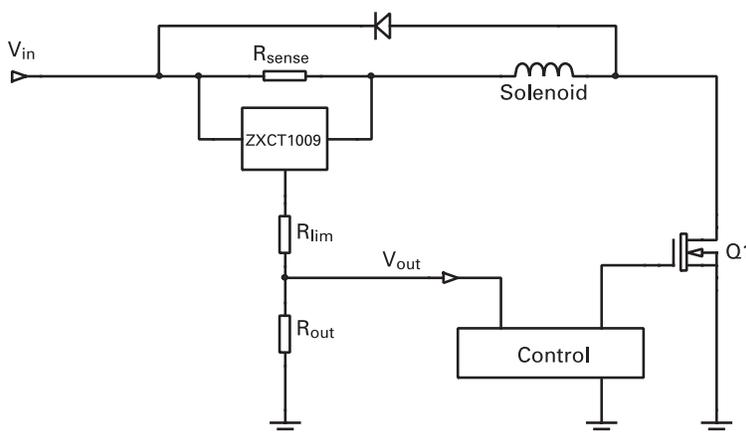

Design Note 77 ISSUE 2 - MARCH 2004

Example

Consider figure 1.0 whereby a 3 Ampere current needs to be measured into a solenoid. 130V transient spikes are present in the system and a 5V output is required to the control IC.

Conditions:

Supply voltage 12 - 16V

$V_{out} = 5V$

$V_{transient} = 130V$

$V_{sense} = 50m\Omega$

The maximum value of the limiting resistor is given by:

$$R_{lim(max)} = \frac{R_{out} [V_{in(min)} - (V_{dp} + V_{out(max)})]}{V_{out(max)}}$$

$R_{lim(max)} = 2.97k\Omega$

Based upon using a 3.3K for R_{out} .

$V_{in(min)}$ = Minimum supply operating voltage

V_{dp} = Dropout voltage

The minimum value is defined with an output voltage of 0V.

$$R_{lim(min)} = \frac{V_{pk} - V_{max}}{I_{pk}}$$

$R_{lim(min)} = 2.75k\Omega$


V_{pk} = Peak voltage transient to be withstood

I_{pk} = Peak output current = 40mA

Short duration high voltage surges therefore can be accommodated using the ZXCT1009, and an additional limiting resistor.

The type of system and surroundings the device is operating in will determine the duration of the transients. Figure 2.0 shows both positive and negative going 130V pulses of short duration which a ZXCT1009 was subjected to. An additional current limiting resistor was added. These simulate possible spike occurrences, which can be seen while measuring the current into a motor or other such inductive loads. The spikes are no greater than milliseconds in duration and no detrimental effects will be suffered to the monitor with the limiting resistor added.

Figure 2 Positive and negative transient spikes

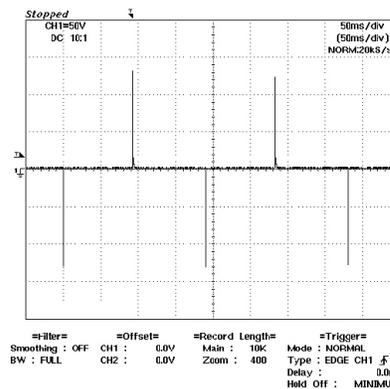

© Zetex plc 2004

Europe	Americas	Asia Pacific	Corporate Headquarters
Zetex GmbH Streitfeldstraße 19 D-81673 München Germany	Zetex Inc 700 Veterans Memorial Hwy Hauppauge, NY 11788 USA	Zetex (Asia) Ltd 3701-04 Metroplaza Tower 1 Hing Fong Road, Kwai Fong Hong Kong	Zetex plc Fields New Road, Chadderton Oldham, OL9 8NP United Kingdom
Telefon: (49) 89 45 49 49 0 Fax: (49) 89 45 49 49 49 europe.sales@zetex.com	Telephone: (1) 631 360 2222 Fax: (1) 631 360 8222 usa.sales@zetex.com	Telephone: (852) 26100 611 Fax: (852) 24250 494 asia.sales@zetex.com	Telephone (44) 161 622 4444 Fax: (44) 161 622 4446 hq@zetex.com

These offices are supported by agents and distributors in major countries world-wide.

This publication is issued to provide outline information only which (unless agreed by the Company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contract or be regarded as a representation relating to the products or services concerned. The Company reserves the right to alter without notice the specification, design, price or conditions of supply of any product or service.

For the latest product information, log on to www.zetex.com

